
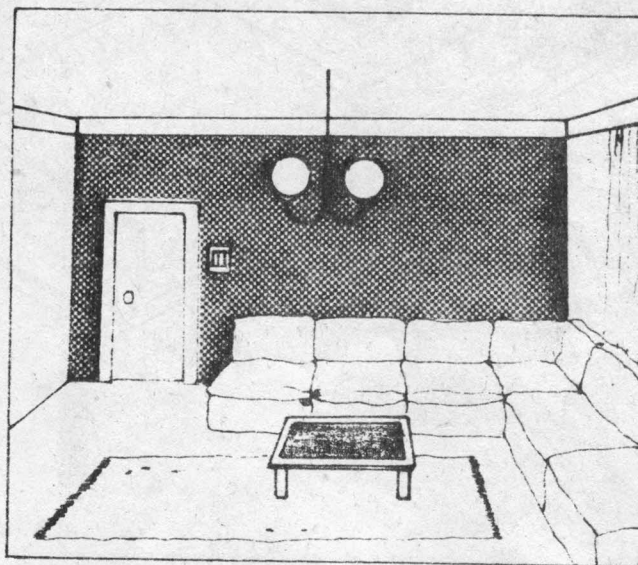



STRUJNO KOLO DVE SIJALICE

ZADATAK: Na osnovu priloženih šema, izometrijskog prikaza i prethodne dve vežbe (u prošlom i sadašnjem broju) poveži strujno kolo. Dve sijalice sa serijskim prekidačem uz izradu potrebnog kontakta na prekidaču i sijaličnog grla.

PRIMENA

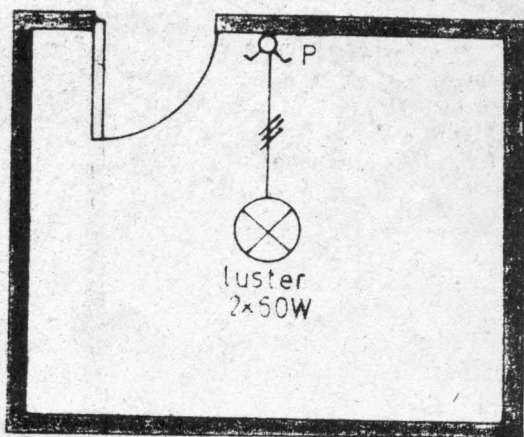


DVOPOLNA ŠEMA

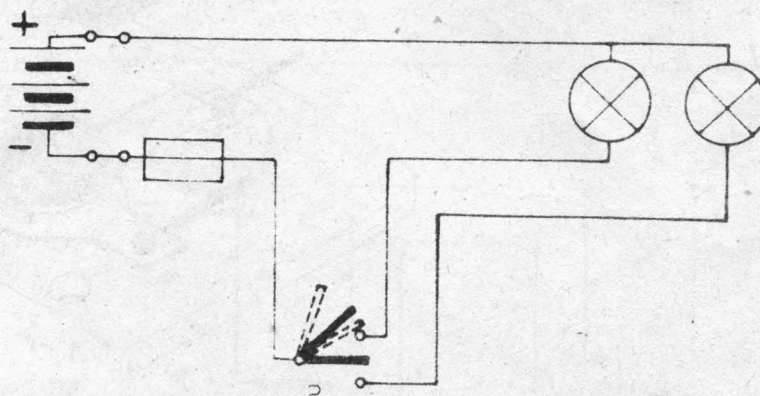



SA SERIJSKIM PREKIDAČEM

prilog
nastavi
VIII razreda

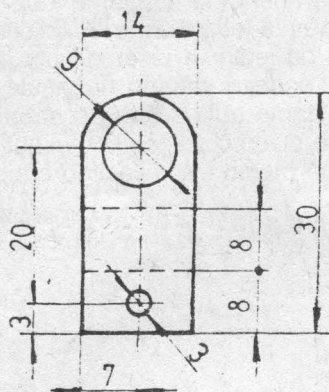


za izradu


al lim 0,8÷1,0 mm

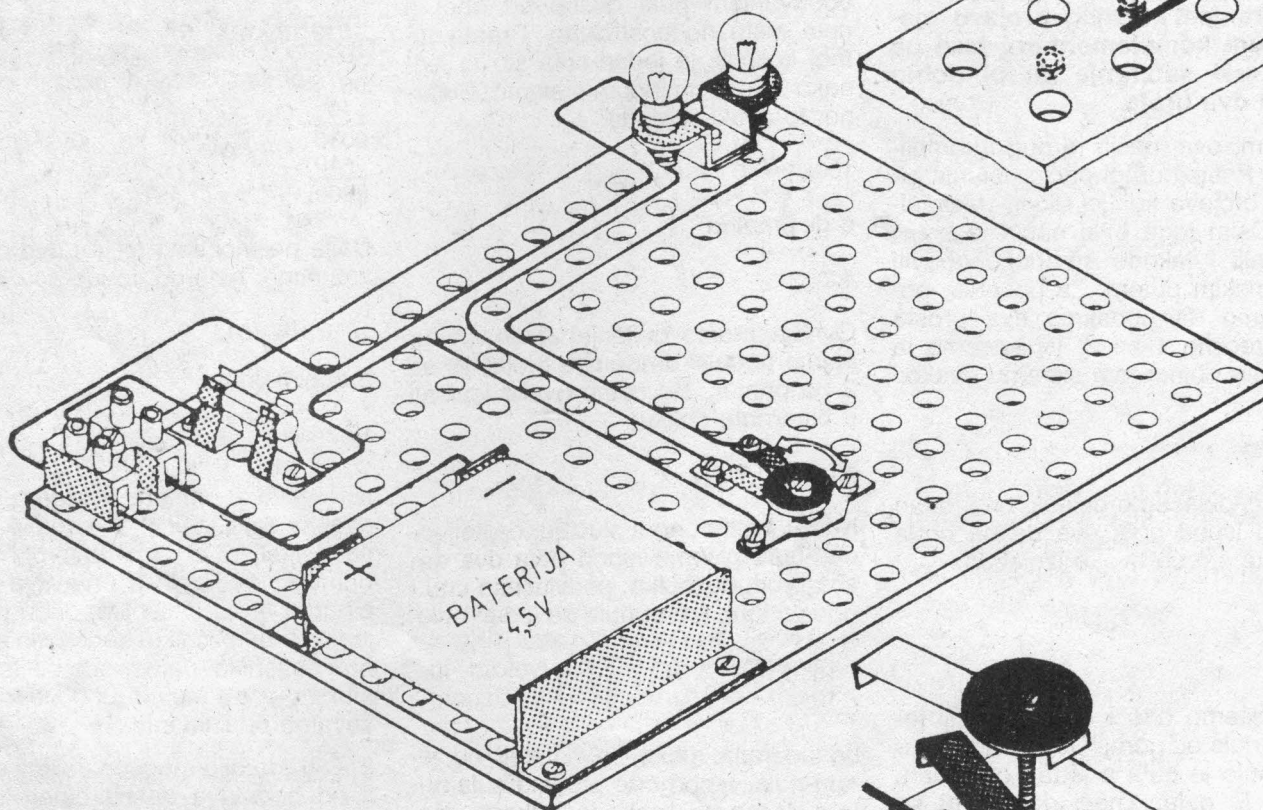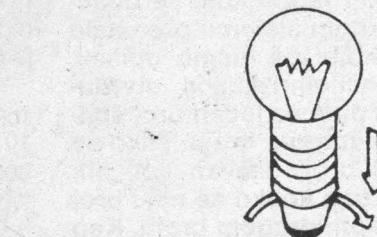

za izradu

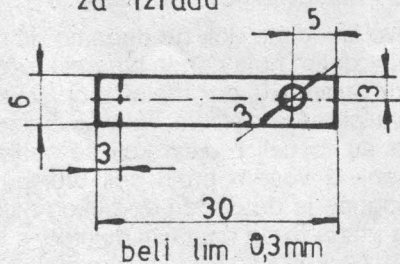

beli lim 0,3 mm

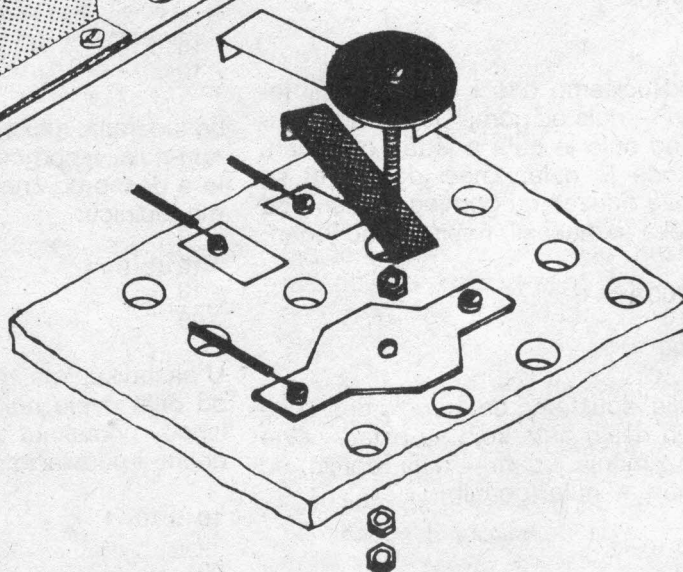

Milan Sanader